

# Assignment 1 — FPGA Lab

Sankala Sreekanth

January 15, 2022

## 1 Question

Reduce the following Boolean expression to its simplest form using K-Map

$$F(X, Y, Z, W) = \sum(0, 1, 6, 8, 9, 10, 11, 12, 15) \quad (1)$$

## 2 Solution

Represent the given Boolean expression in K-Map and follow the K-Map rules to reduce the given Boolean form to simplest form

		ZW			
		00	01	11	10
XY	00	1	1	0	0
	01	0	0	0	1
	11	1	0	1	0
	10	1	1	1	1

$$F(X, Y, Z, W) = \bar{Y}.\bar{Z} + X.\bar{Y} + X.\bar{Z}.\bar{W} + X.Z.W + \bar{X}.Y.Z.\bar{W} \quad (2)$$

## 3 Implimentation using NAND gate

$$F(X, Y, Z, W) = \overline{\overline{\bar{Y}.\bar{Z}} + \overline{X.\bar{Y}} + \overline{X.\bar{Z}.\bar{W}} + \overline{X.Z.W} + \overline{\bar{X}.Y.Z.\bar{W}}} \quad (3)$$

$$F(X, Y, Z, W) = \overline{\overline{\bar{Y}.\bar{Z}} + \overline{X.\bar{Y}} + \overline{X.\bar{Z}.\bar{W}} + \overline{X.Z.W} + \overline{\bar{X}.Y.Z.\bar{W}}} \quad (4)$$